

Experiment 4 Lab Report
EEE3342C - 00012

Yousef Awad

March 2025

Contents

Equipment	2
Objective	2
Part 1: Half/Full Adder	2
Half Adder	2
Full Adder	4
Part 2: 8-Bit Ripple Carry Adder	6
Part 3: Carry Look-Ahead Adder	8
Part 4: 32-bit Adder and Subtractor	11
Conclusion	14

Equipment

For this experiment a computer running Linux 6.12.13 was used alongside the Xilinx Vivado 2024.2 software, alongside an FPGA board, the BASYS 3 development board. The board specifically only used to ensure the simulation by the Vivado software was accurate in the real world, as well as to verify the simulation software wasn't incorrect.

Objective

Part 1: Half/Full Adder


Half Adder

The circuit given for this part was the following:

$$\neg[(A \wedge B) \vee \neg(C \vee D)]$$

Of which has the following given schematic:

Figure 1: Schematic for Half Adder

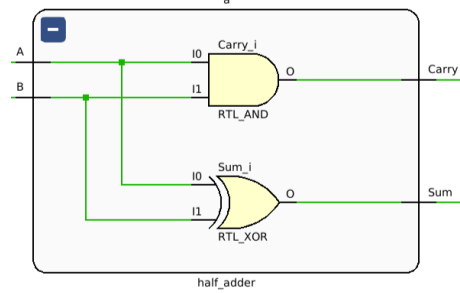

And when compiled into a truth table with the inputs of A, B, and an output of Carry, would be the following:

Truth Table for Half Adder

<i>A</i>	<i>B</i>	<i>Output</i>	<i>Carry</i>
<i>F</i>	<i>F</i>	<i>F</i>	<i>F</i>
<i>F</i>	<i>T</i>	<i>T</i>	<i>F</i>
<i>T</i>	<i>F</i>	<i>T</i>	<i>F</i>
<i>T</i>	<i>T</i>	<i>F</i>	<i>T</i>

And when written up in verilog, has the following text:

```

1 module half_adder(
2     input A, B,
3     output Sum, Carry
4 );
5
6 assign Sum = A ^ B;
7 assign Carry = A & B;
8
9 endmodule

```

And when tested, used the following testbench, after reading through part 1 of the experiment manual:


```

1 module testbench();
2     parameter numin = 2;
3     integer i;
4     reg[numin - 1:0] count;
5
6     reg a, b;
7     wire carry, sum;
8
9     half_adder UUT(.A(a), .B(b), .Carry(carry), .Sum(sum));
10
11
12     initial begin
13         count = 0;
14         for ( i = 0; i < 2**numin; i = i + 1 ) begin
15             assign a = count[1];
16             assign b = count[0];
17
18             count = count + 1;
19             #10;
20         end
21     end
22
23 endmodule

```

And, when simulated to confirm the truth table above to be true or false, it gave out the following waveform:

Figure 2: Waveform for the Half-Adder

 


Of which perfectly shows that the truth table compiled above for the circuit is accurately shown in the simulation on Vivado. To ensure, even further, I then pushed the bitstream generated onto the BASYS board to manually enter and double check the simulation/truth table proper by flicking every possible combination.

Full Adder

The circuit schematic given for this part was the following:

Figure 3: Schematic for Full Adder

 

And when written up in verilog, has the following text:

```

1 module full_adder(
2     input A, B, CarryIN,
3     output Sum, CarryOUT
4 );
5
6 wire carry1, carry2, sum1;
7
8 half_adder a(.A(A), .B(B), .Carry(carry1), .Sum(sum1));
9 half_adder b(.A(CarryIN), .B(sum1), .Sum(Sum), .Carry(
10     carry2));
11
12 assign CarryOUT = carry1 | carry2;
13 endmodule

```

And when tested, used the following testbench, after reading through part 1 of the experiment manual:


```

1 module testbench();
2     parameter numin = 2;
3     integer i;
4     reg[numin - 1:0] count;
5
6     reg a, b, carryIN;
7     wire carry, sum;
8
9     full_adder UUT(.A(a), .B(b), .CarryIN(carryIN), .
10         CarryOUT(carry), .Sum(sum));
11
12     initial begin
13         count = 0;
14         for ( i = 0; i < 2**numin; i = i + 1 ) begin
15             assign a = count[1];
16             assign b = count[0];
17             assign carryIN = 0;
18
19             count = count + 1;
20             #10;
21         end
22     end
23 endmodule
24

```

And, when simulated, it gave out the following correct waveform:

Figure 4: Waveform for the Half-Adder

 


To ensure, even further past the given truth table in lab report, I then pushed the bitstream generated onto the BASYS board to manually enter and double check the simulation proper by flicking every possible combination.

Part 2: 8-Bit Ripple Carry Adder

The schematic was designed as following:

Figure 5: Schematic for 8 Bit Ripple Carry Adder

 

And when written up in verilog, has the following text:

```

1 module eight_bit_ripple_adder(
2     input [7:0] A, B,
3     input CarryIN,
4     output [7:0] Sum,
5     output CarryOUT
6 );
7
8 wire [8:0] carry;
9
10 assign carry[0] = CarryIN;
11
12 genvar i;
13
14 generate
15     for ( i = 0; i < 8; i = i + 1 ) begin
16         full_adder a(.A(A[i]), .B(B[i]), .CarryIN(carry[
17             i]), .CarryOUT(carry[i + 1]), .Sum(Sum[i]));
18     end
19 endgenerate
20
21 assign CarryOUT = carry[8];
22 endmodule

```

And when tested, used the following testbench, after reading through part 1 of the experiment manual:

```

1 module testbench_part2();
2     parameter numin = 8;
3
4     reg[numin - 1:0] a, b;

```


```

5      reg carryIN;
6      wire[numin - 1:0] sum;
7      wire carryOUT;
8
9      eight_bit_ripple_adder UUT(.A(a), .B(b), .CarryIN(
10         carryIN), .CarryOUT(carryOUT), .Sum(sum));
11
12      initial begin
13          assign a = 8'b11001011;
14          assign b = 8'b10101010;
15          assign carryIN = 0;
16          #10;
17          assign carryIN = 1;
18          #10;
19          assign a = 0;
20          assign b = 0;
21          assign carryIN = 0;
22      end
23 endmodule

```

And, when simulated to confirm the addition of 170 and 203 (assuming it is unsigned) above to be 0x75 Carry 1 as it overflows and switches sign, it gave out the following waveform:

Figure 6: Waveform for Addition of 0x170 and 0x203

 


Of which perfectly shows the correct result to be 0x75 or 0x76 of which is in binary either 01001011 or 01001100 and in decimal is 117, depending on the carry in value with a carry out of 1 meaning it overflowed.

Part 3: Carry Look-Ahead Adder

The schematic was designed as following:

Figure 7: Schematic for 8 Bit Carry Look-Ahead Adder

 

And when written up in verilog, has the following text:

```

1 module eight_bit_carry_look_adder( // part 3
2     input[7:0] Num1, Num2,
3     input CarryIN,
4     output[7:0] Sum,
5     output CarryOUT
6 );
7 // why use carry look ahead adders?
8 // this gets rid of the propogation delay and therefore is
9 // "faster", of which adds in parallel instead of
10 // sequentially.
11 // this, however, uses a lot more gates to be used and is
12 // therefore more area intensive.
13 wire[7:0] carryGenerate, carryPropagate, carryTemp;
14 genvar i; // temporary variable i
15
16 // logic for carry look adders
17 assign carryGenerate = Num1 & Num2;
18 assign carryPropagate = Num1 ^ Num2;
19
20 assign carryTemp[0] = CarryIN;
21 generate
22     for ( i = 1; i < 8; i = i + 1) begin
23         assign carryTemp[i] = carryGenerate[i - 1] | (
24             carryPropagate[i - 1] & carryTemp[i - 1]);
25     end
26 endgenerate
27
28 // addition logic proper
29 generate
30     full_adder a(.A(Num1[0]), .B(Num2[0]), .CarryIN(CarryIN),
31         .CarryOUT(), .Sum(Sum[0]));
32     for (i = 1; i < 8; i = i + 1) begin
33         full_adder a(.A(Num1[i]), .B(Num2[i]), .CarryIN(
34             carryTemp[i]), .CarryOUT(), .Sum(Sum[i]));
35     end
36 endgenerate
37
38 assign CarryOUT = carryTemp[7];
39 endmodule

```



```

29     end
30   endgenerate
31
32   assign CarryOUT = carryTemp[7];
33
34 endmodule

```

And when tested, used the following testbench:


```

1 module testbench_part3();
2   reg [7:0] Num1, Num2;
3   reg CarryIN;
4
5   wire [7:0] Sum;
6   wire CarryOUT;
7
8   eight_bit_carry_look_adder instance_1(.Num1(Num1), .Num2(
9     Num2), .CarryIN(CarryIN), .CarryOUT(CarryOUT), .Sum(Sum
10    ));
11
12   initial begin
13     Num1 = 8'b11001011;
14     Num2 = 8'b10101010;
15     CarryIN = 0;
16     #10;
17   end
18 endmodule

```


And, when simulated to confirm the addition of $11001011 + 10101010$ (assuming it is unsigned), it gave out the following waveform:

Figure 8: Waveform Addition CLA

 

Of which perfectly shows the correct result to be when compared to the addition for the Ripple Carry Adder waveform below:

Figure 9: Waveform Addition RCA

 


And, since both waveforms are the exact same, means that the verilog code proper is, in effect, also the same, at least results wise. Area and latency wise, they are different.

Part 4: 32-bit Adder and Subtractor

The schematic was designed as following:

Figure 10: Schematic for 32 Bit Adder/Subtractor

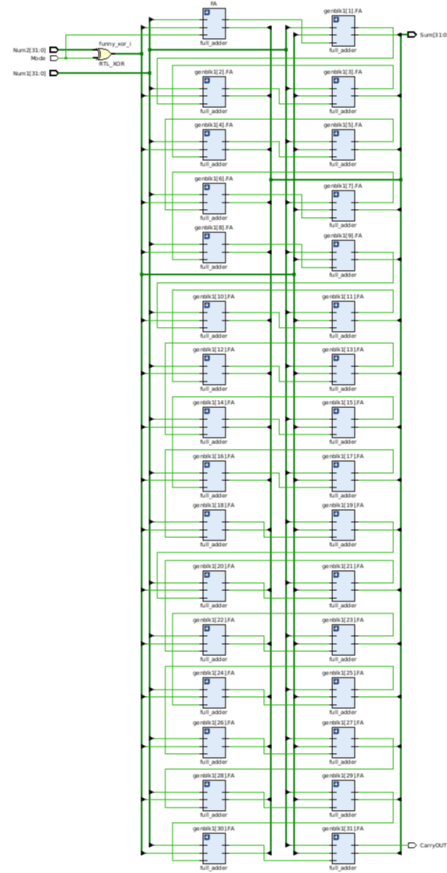

And when written up in verilog, has the following text:

```

1 module thirtytwo_bit_multi_adder( // part 4
2     input [31:0] Num1, Num2,
3     input Mode, // carryIN is the mode for reference
4     output [31:0] Sum,
5     output CarryOUT
6 );
7
8 wire [31:0] funny_xor, carry;
9
10 assign funny_xor = Num2 ^ {32{Mode}}; // xo's Num2 with
    the mode for 2's complement subtraction.

```

```

11
12     genvar i;
13
14     generate
15         full_adder FA(.A(Num1[0]), .B(funny_xor[0]), .CarryIN(
16             Mode), .Sum(Sum[0]), .CarryOUT(carry[0]));
17         for (i = 1; i < 32; i = i + 1) begin
18             full_adder FA(.A(Num1[i]), .B(funny_xor[i]), .CarryIN(
19                 carry[i - 1]), .Sum(Sum[i]), .CarryOUT(carry[i]));
20         end
21     endgenerate
22
23     assign CarryOUT = carry[31];
24
25 endmodule

```

And when tested, used the following testbench:


```

1 module testbench_part4();
2     reg[31:0] num1, num2;
3     reg mode;
4
5     wire [31:0] sum;
6     wire carryout;
7
8     // CarryIN is the mode (0 for addition; 1 for subtractions
9     // )
10    thirtytwo_bit_multi_adder UUT(.Num1(num1), .Num2(num2), .
11        Mode(mode), .CarryOUT(carryout), .Sum(sum));
12
13    initial begin
14        mode = 0;
15        num1 = 32'd50;
16        num2 = 32'd25;
17        #10;
18
19        mode = 1;
20        num1 = 32'd50;
21        num2 = 32'd25;
22        #10;
23    end
24
25 endmodule

```

And, when simulated to confirm the addition, and subtraction, of 50 and 25, it gave out the following waveform:

Figure 11: Waveform Addition/Subtraction Waveform

 

And of which compiles to the following truth table showing what the "Mode" change does to the number result:

Truth Table for 32 Bit Adder/Subtractor

<i>A</i>	<i>B</i>	<i>Mode</i>	<i>Result</i>
50	25	<i>F</i>	75
50	25	<i>T</i>	25

Of which you can see, the "mode" simply switches the base addition of the decimal values of 50 and 25, to, when flicked to True/1, to being the subtraction of the second number to the first.

Now, while in this testcase example, we utilized a simple array of full-adders, we also could use an array of 4 Ripple Carry Adders (as those are more optimized for power and therefore area costs, unlike latency), and would therefore be superior to the schematic and code above, at least for the goals of the assignment given. Alongside this, at least with the current design that I've described in verilog above, it is a happy medium between all modes due to the fact that it is the simplest form of how one could make a 32 bit adder, of which is just a sequential chain of adders feeding into one another their carryINs and carry-OUTs. And, yes, while there is latency involved, it would also, at least, provide its purpose as a general run of the mill 32-bit adder/subtractor.

Conclusion

Now, in conclusion, we have learned the following things, listed of course in paragraph order in chronological order of this report.

First we learned on how to make a full adder, of which takes in 2 half adders, of which comprise of 2 gates (one AND and one XOR), and have an additional OR making it a total of 5 gates total per full adder.

Secondly, we learned that there are tradeoffs to how we design digital systems as a computer hardware engineer. Of which are specifically the timing of the system (also known as latency of the calculation), the area/size of the actual hardware proper, the performance/speed of the hardware (as well as if it is running in parallel or sequential), and finally the power it consumes as a component. Alongside this, we learned of 2 types of scalable multi-bit adders: the Ripple Carry Adder, and the Carry Look-Ahead Adder. Of which have the following pro's and con's:

The Ripple Carry Adder has the pro that it's simple to make and use, as well as uses less area and power compared to the Carry Look-Ahead Adder. It, however, loses out in its speed as well as timing, due to the fact that every bit in the addition requires the computation of the bit before it before it can continue, meaning that as you scale to 32 bits or even 64, significant delays occur.

For Carry Look-Ahead Adders, it is more performance and timing efficient than standard adder chains, and even the Ripple Carry Adder, BUT has a problem in that it is much more complex, as well as takes up much more power due to that complexity (due to its 56 gates compared to the Ripple Carry Adder's 40 gates), alongside its area impact, making it useful only for large scale additions and subtractions, that must be completed as fast as possible.